

CMSC 411 | Computer Architecture

Lecture 11: **Multiplier Design**

Dr. Ergun Simsek



Facit C1-13

<https://www.youtube.com/watch?v=zJ3q4zjCKnM>

Overview

Previous Lecture

- Constructing an Arithmetic Logic Unit
- Addition, subtraction, slt, and branching

This Lecture

- Algorithms for multiplying unsigned numbers
- Booth's algorithm for signed number multiplication
- Multiple hardware design for integer multiplier

How Humans Multiply

Multiplicand

1000

m bits

Multiplier

x1001

n bits

1000

0000

0000

1000

+

Product

0 1001000

m+n bits

Computer does the almost
same thing

Binary makes things easy


0 => place 0 (0 x multiplicand)

1 => place a copy (1 x multiplicand)

Unsigned mult has no
overflow risk, so let's forget
about the sign problem and
focus on some mult designs

How would you design it?

Unsigned Combinational Multiplier

 


- Stage i accumulates $A * 2^i$ if $B_i == 1$
- At each stage shift A left ($\times 2$)
- Use next bit of B to determine whether to add in shifted multiplicand
- Accumulate 2n bit partial product at each stage

Unsigned shift-add multiplier (version 1)


Assume we have a

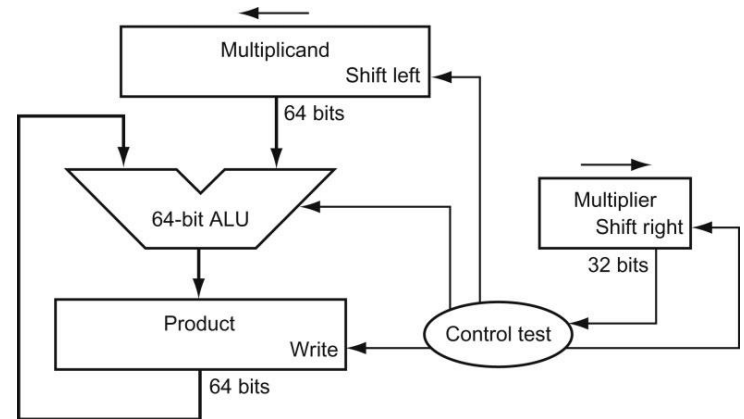- 64-bit **multiplicand** register,
- 64-bit ALU,
- 64-bit product register, and
- 32-bit **multiplier** register




- The 32-bit value of the **multiplicand** starts in the right half of the 64-bit register
- The **multiplier** is shifted in the opposite direction of the **multiplicand** shift
- The product register starts with an initial value of zero
- Control decides when to shift the **multiplicand** and the **multiplier** registers and when to write new value into the product register

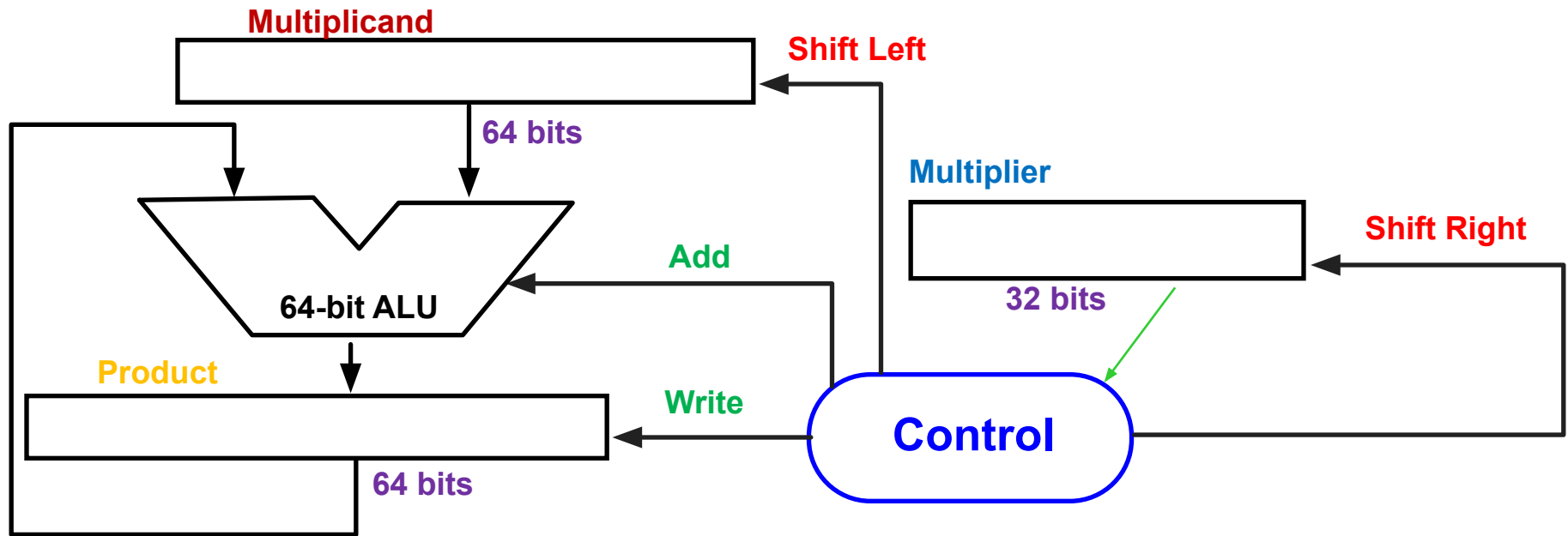Unsigned shift-add multiplier (version 1)



Multiplier = Datapath + Control

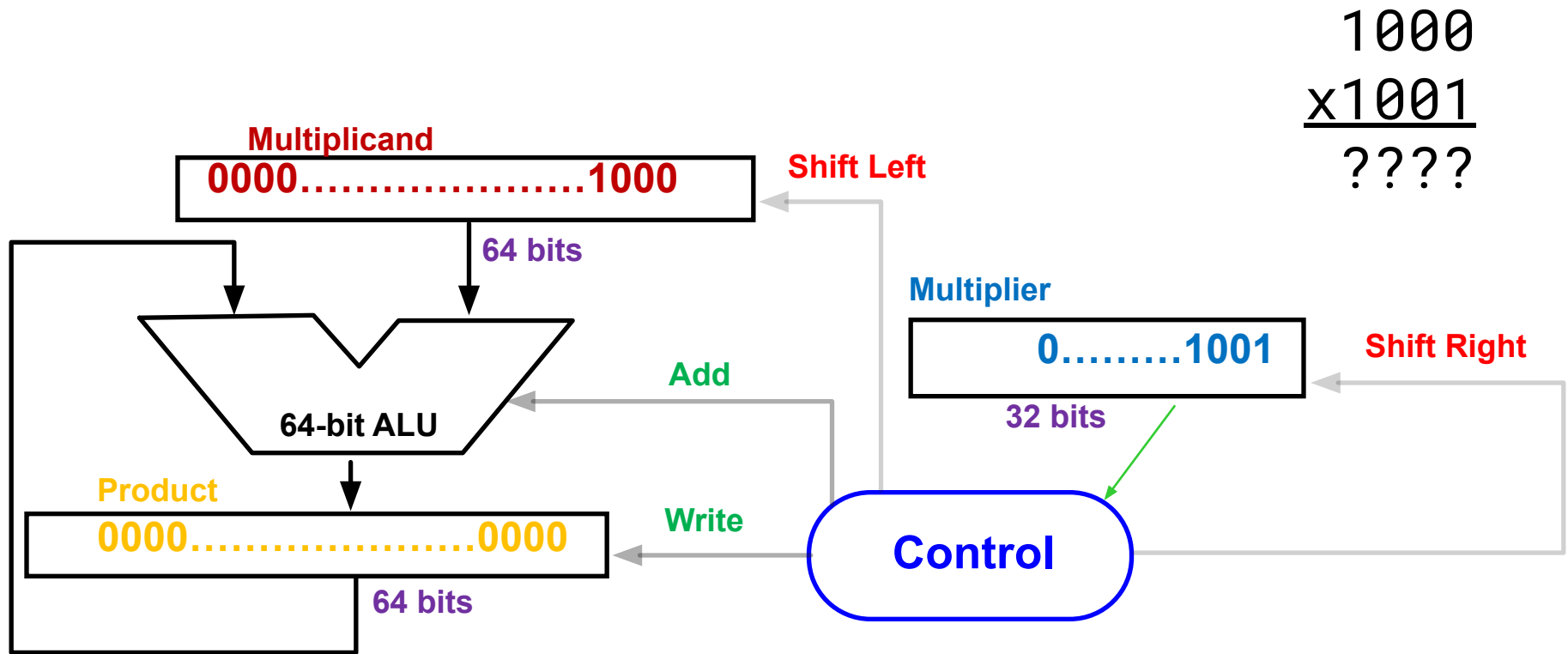Unsigned shift-add multiplier (version 1)




Multiplier = Datapath + Control

Multiplicand 1000
Multiplier x1001


Product 00000000

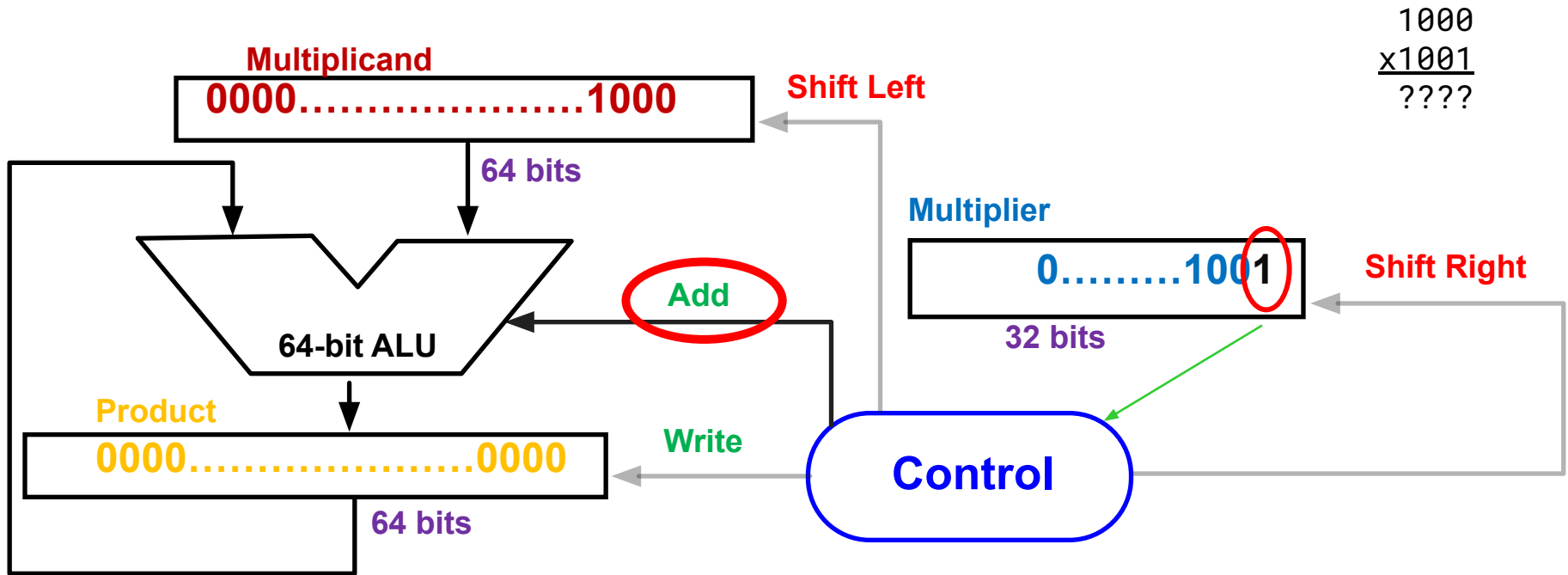Unsigned shift-add multiplier (version 1)




Multiplier = Datapath + Control

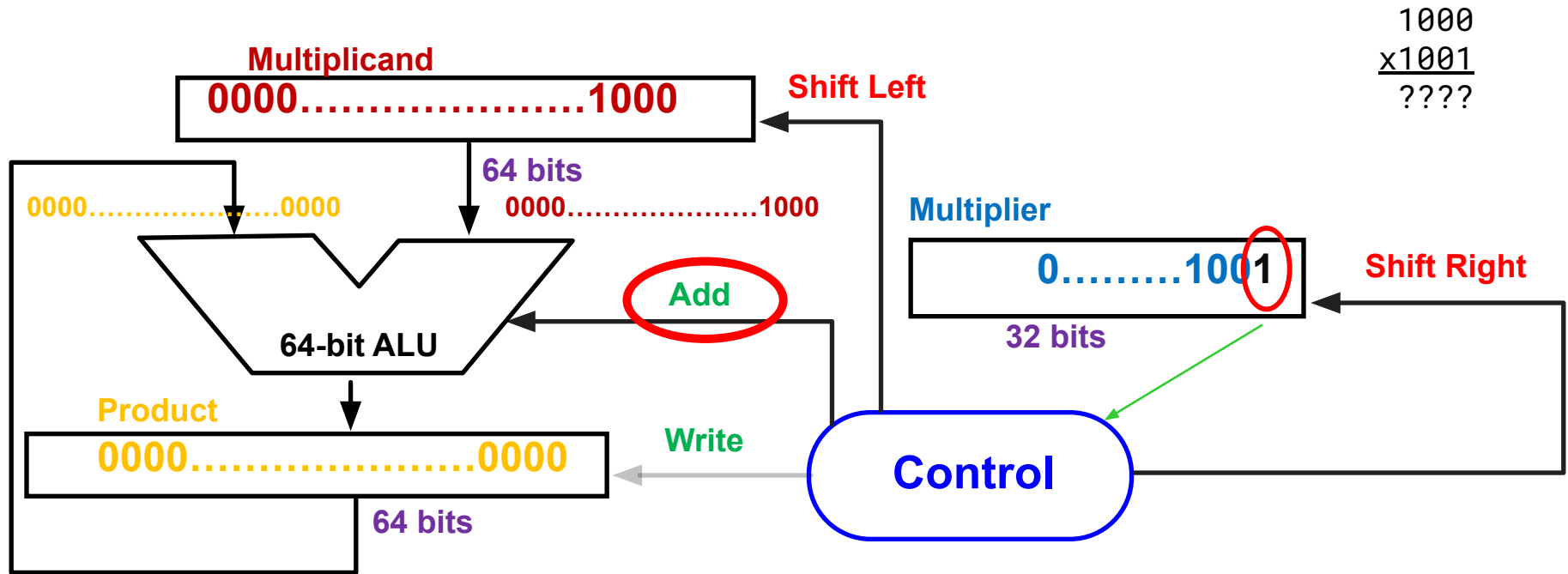Unsigned shift-add multiplier (version 1)




Multiplier = Datapath + Control

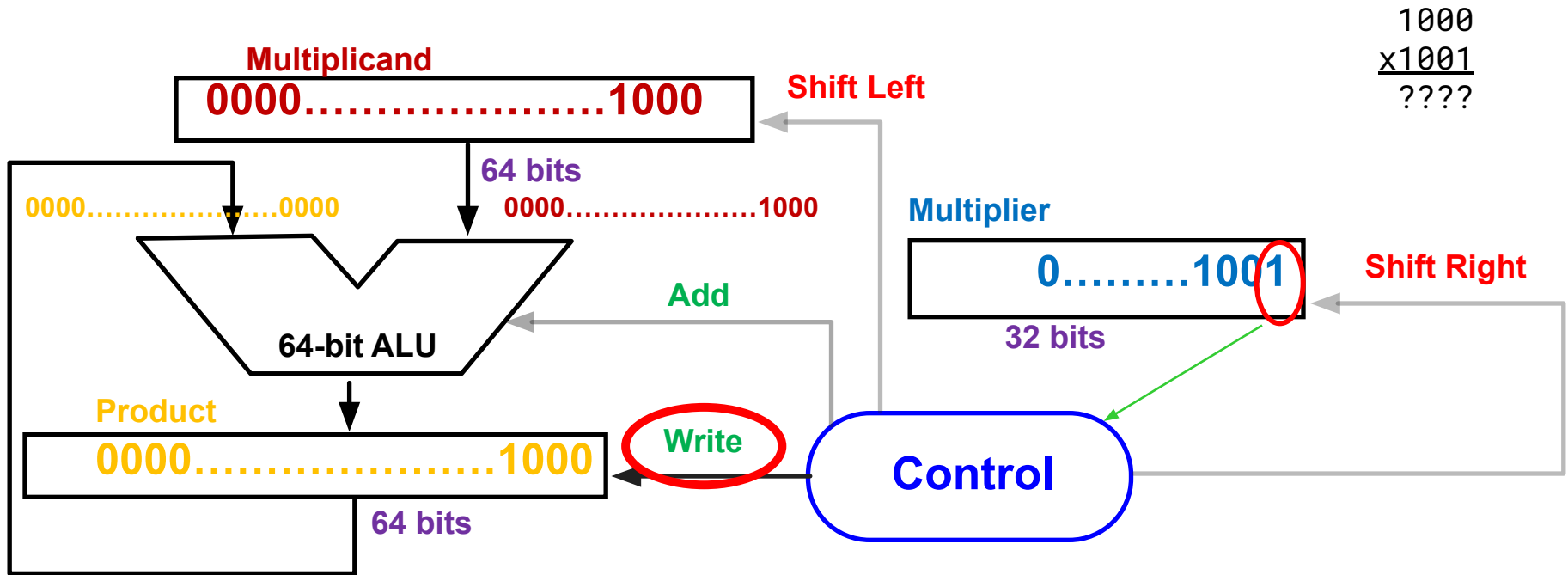Unsigned shift-add multiplier (version 1)




Multiplier = Datapath + Control

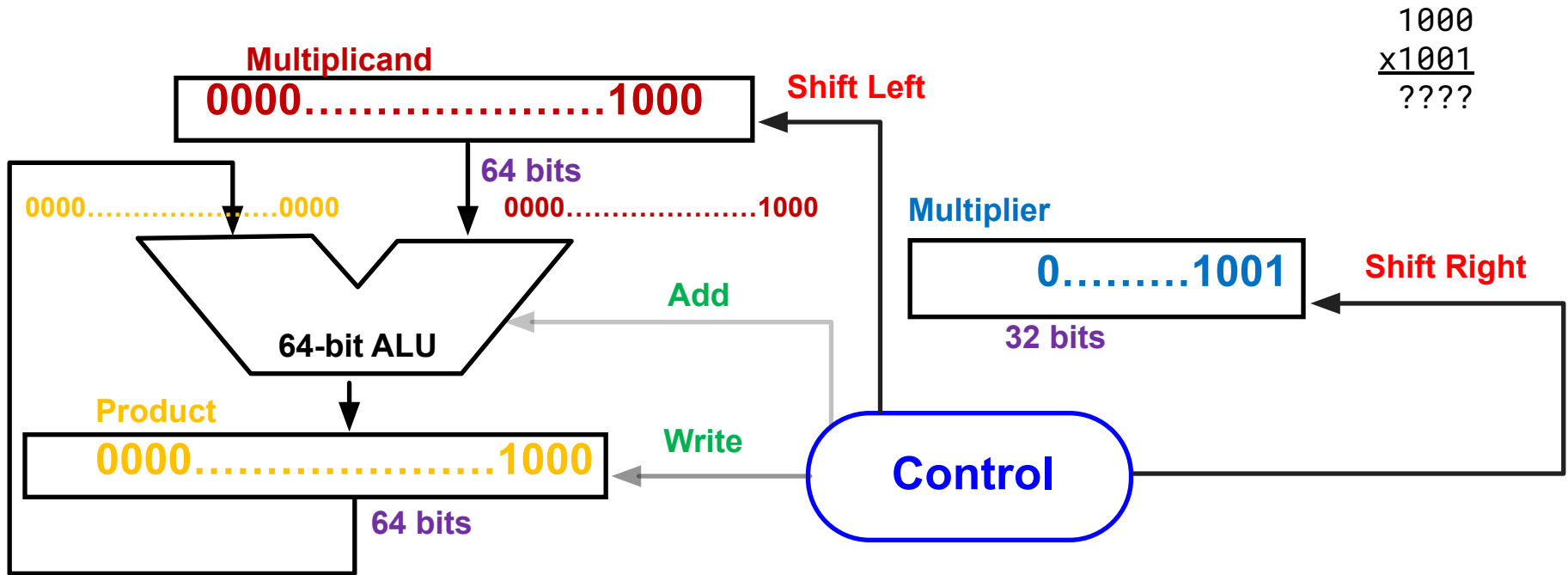Unsigned shift-add multiplier (version 1)




Multiplier = Datapath + Control

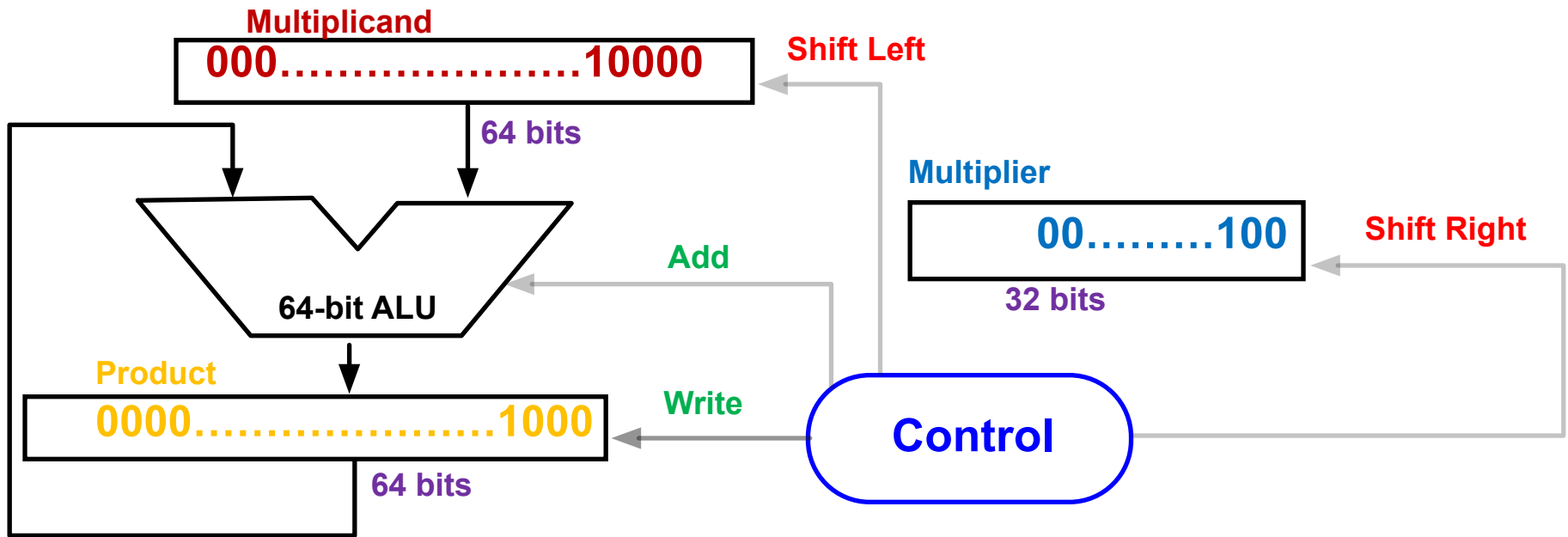Unsigned shift-add multiplier (version 1)




Multiplier = Datapath + Control

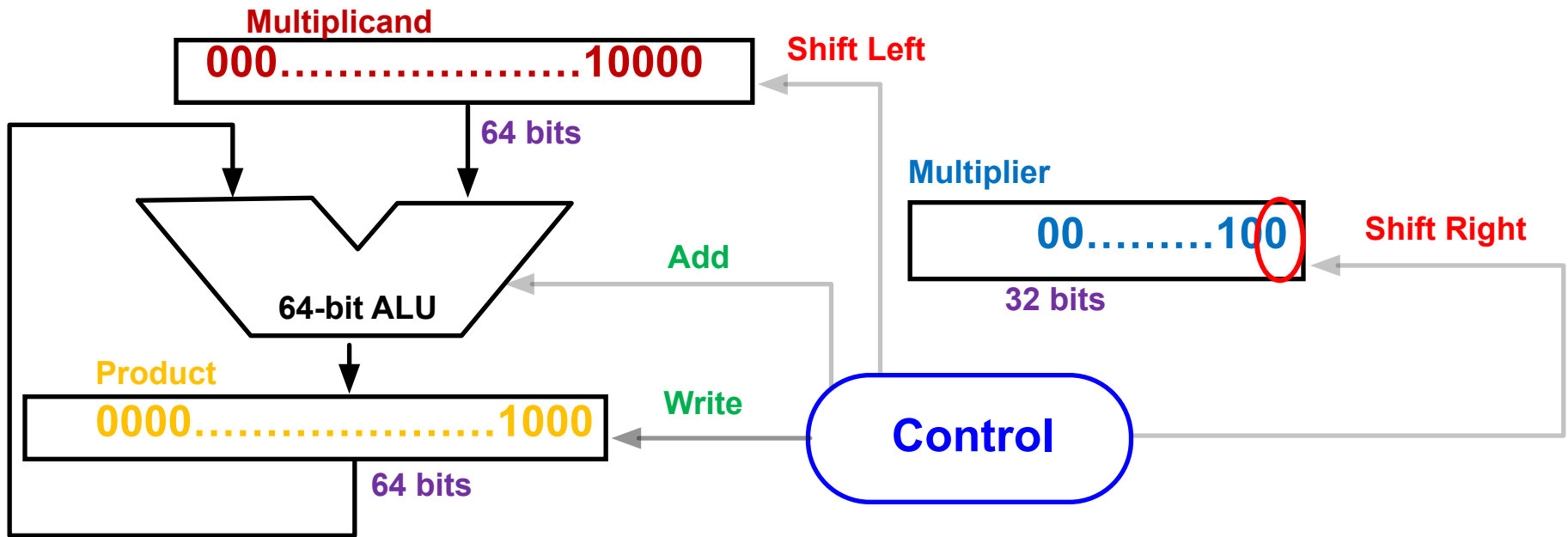Unsigned shift-add multiplier (version 1)




Multiplier = Datapath + Control

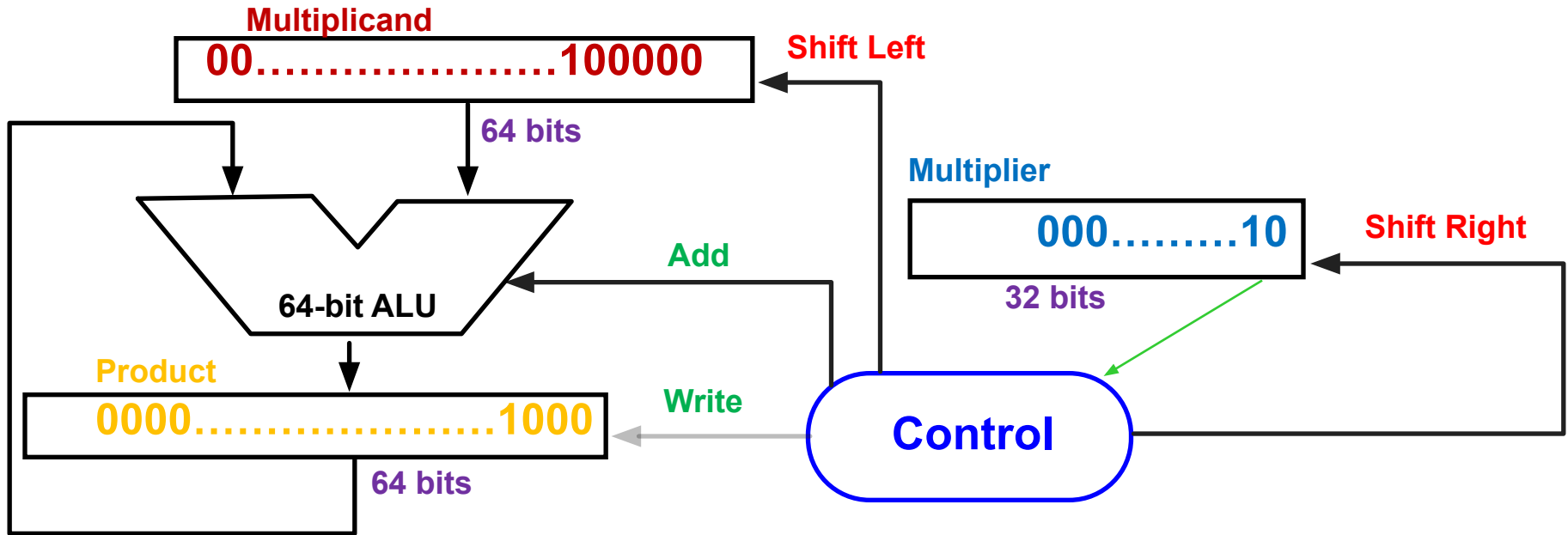Unsigned shift-add multiplier (version 1)




Multiplier = Datapath + Control

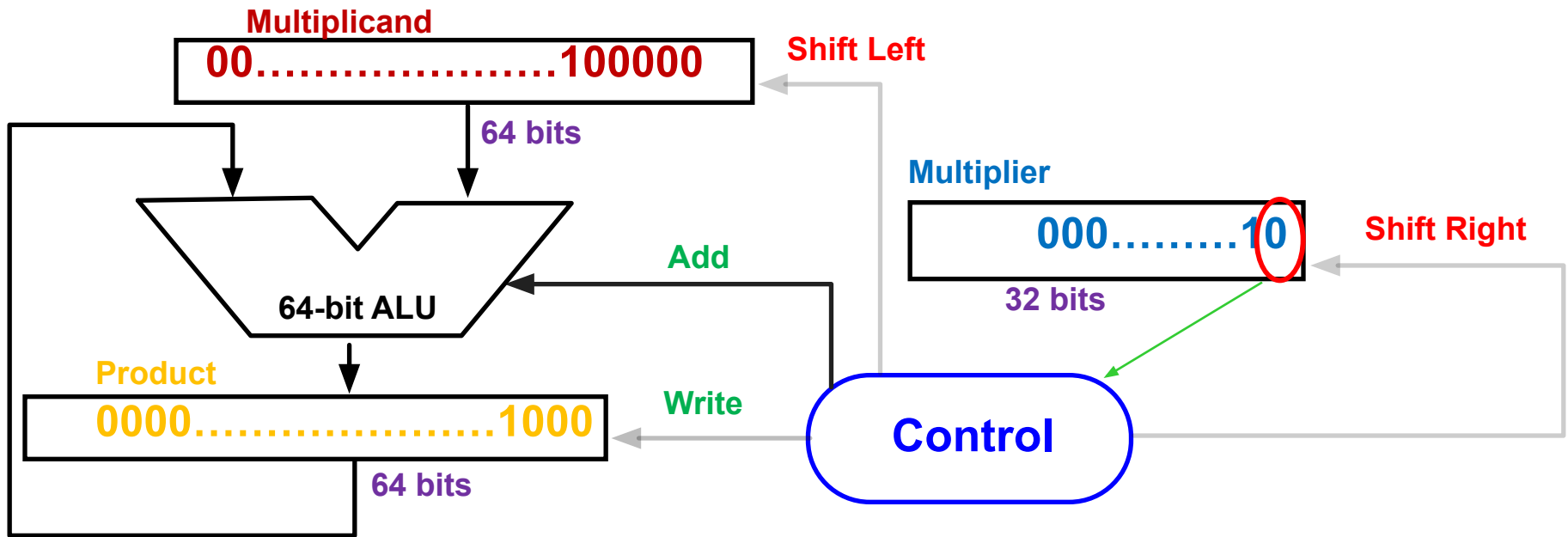Unsigned shift-add multiplier (version 1)




Multiplier = Datapath + Control

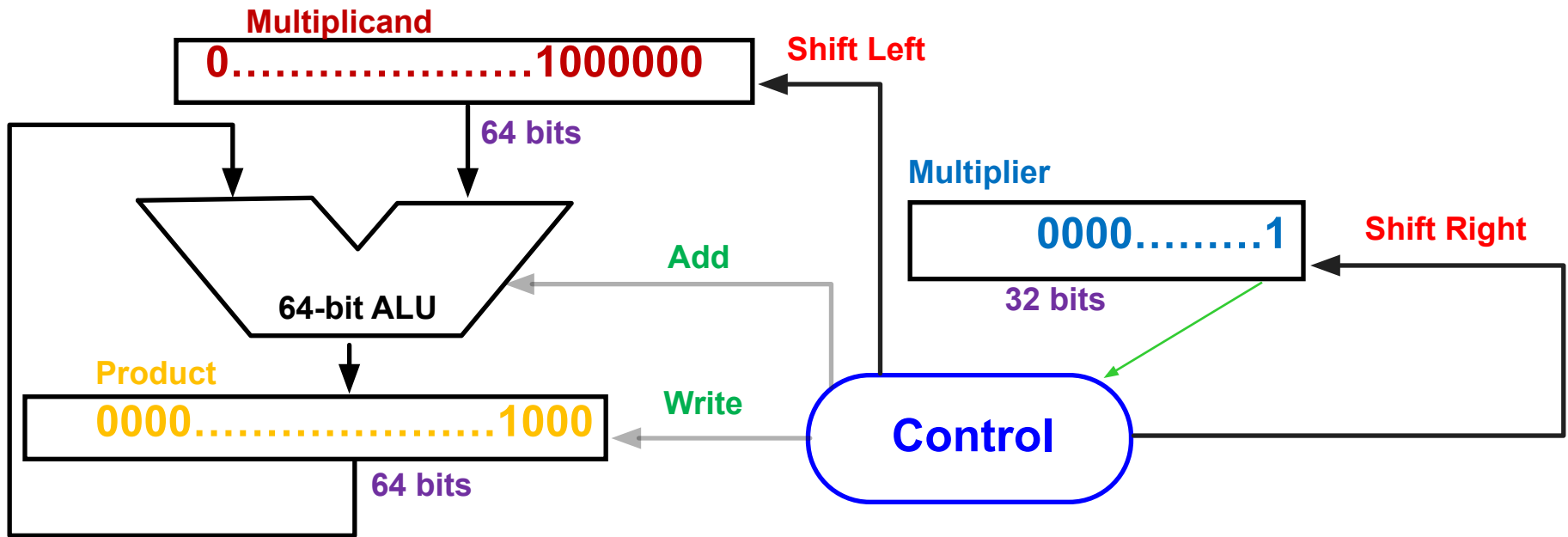Unsigned shift-add multiplier (version 1)




Multiplier = Datapath + Control

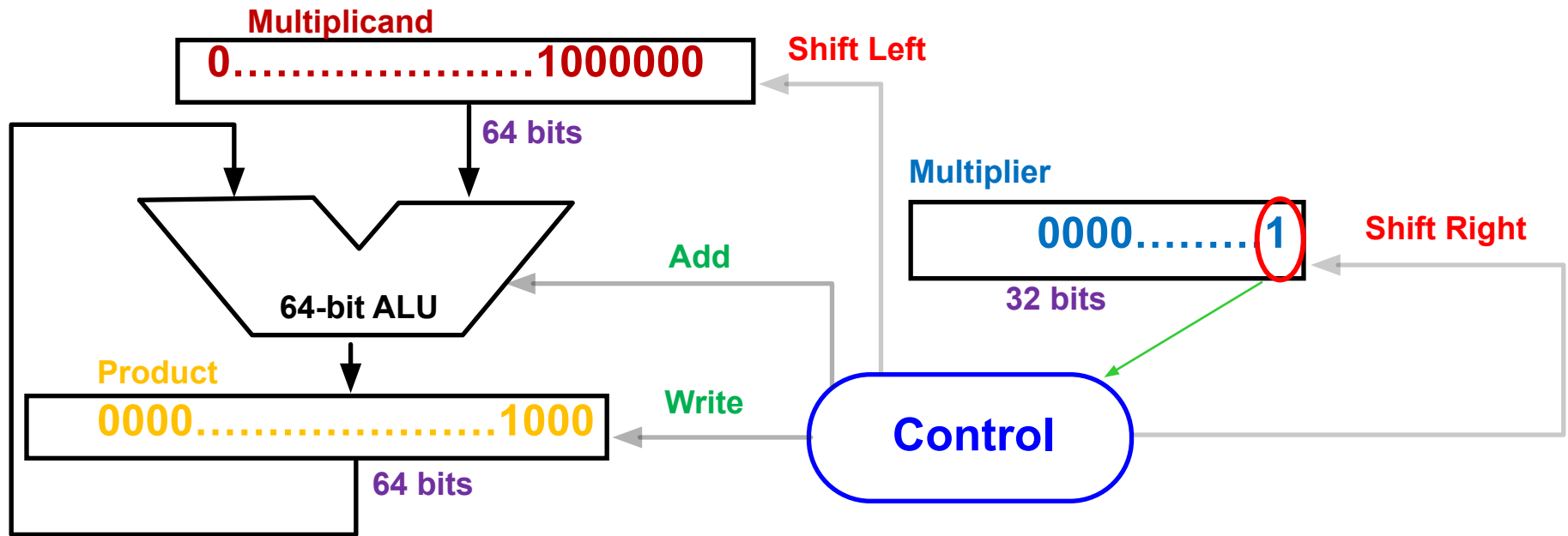Unsigned shift-add multiplier (version 1)




Multiplier = Datapath + Control

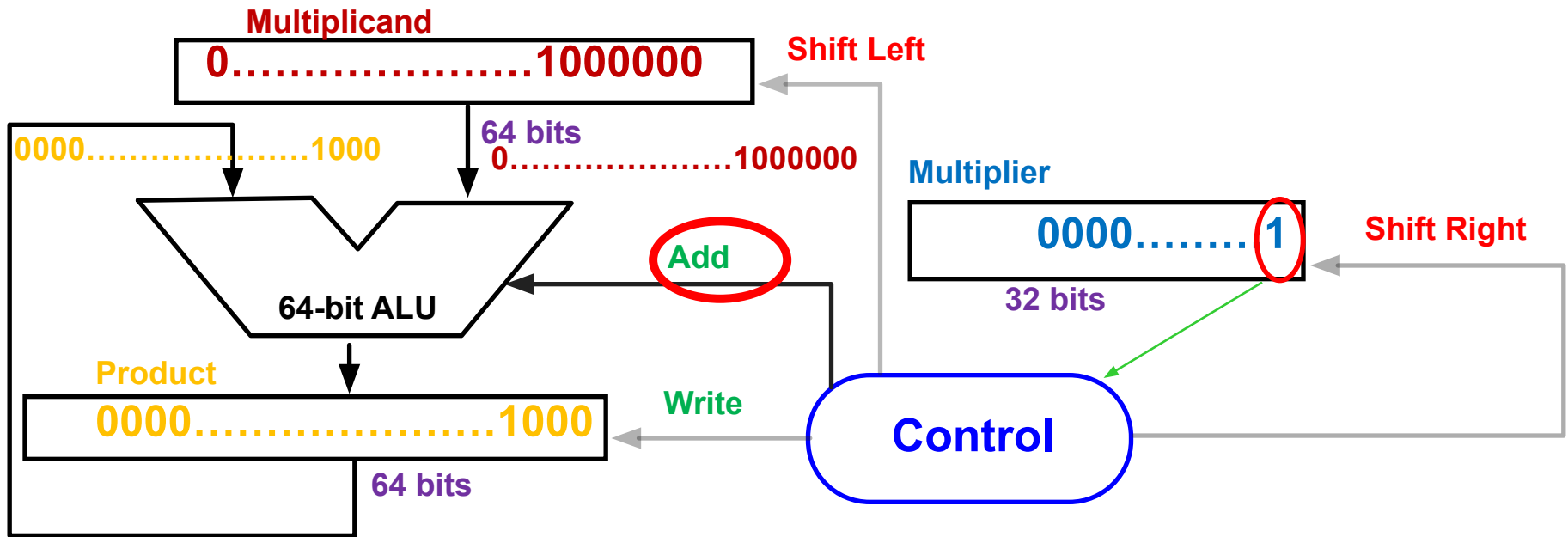Unsigned shift-add multiplier (version 1)




Multiplier = Datapath + Control

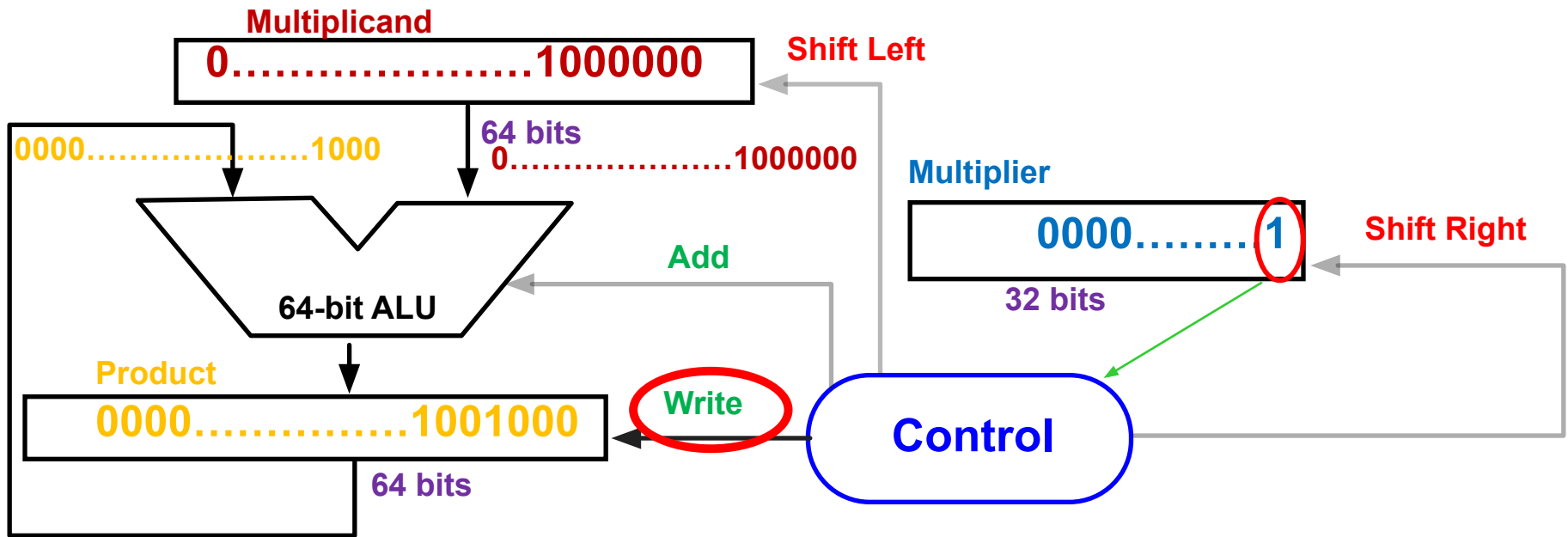Unsigned shift-add multiplier (version 1)



Multiplier = Datapath + Control

 
Unsigned shift-add multiplier (version 1)



Multiplier = Datapath + Control

Multiply Algorithm Version 1

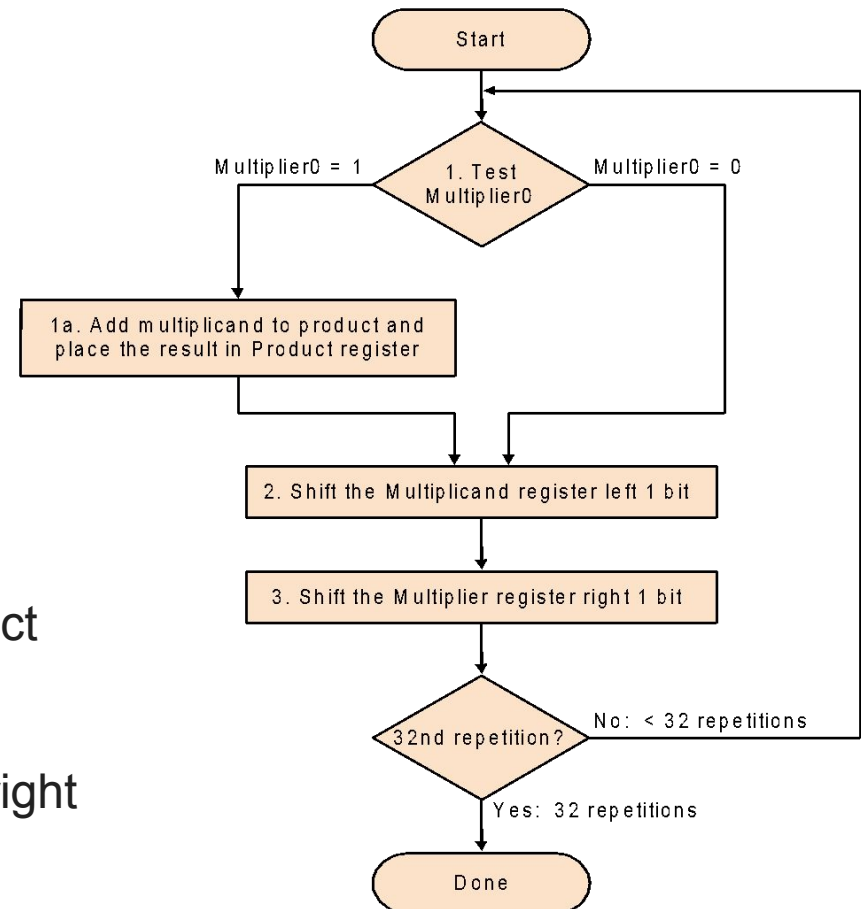
Multiplying two n -bit numbers needs a maximum of $2n^2$ addition operations mostly for adding zeros




- If the least significant bit of the multiplier is
 - 1, then add the multiplicand to the product
 - 0, then go to the next bit
- Shift the multiplicand left and the multiplier right
- Repeat for 32 times

Multiply Hardware Version 2

- Since half of the 64-bit **Multiplicand** are zeros, a 64-bit ALU looks wasteful in the first version of multiplier
- This version uses only 32-bit **Multiplicand** register, 32-bit ALU, 64-bit **Product** register, and 32-bit **Multiplier** register
- Since the least significant bits of the product would not change, the product could be shifted to the right instead of shifting the multiplicand
- The most significant 32-bits would be used by the ALU as a result register

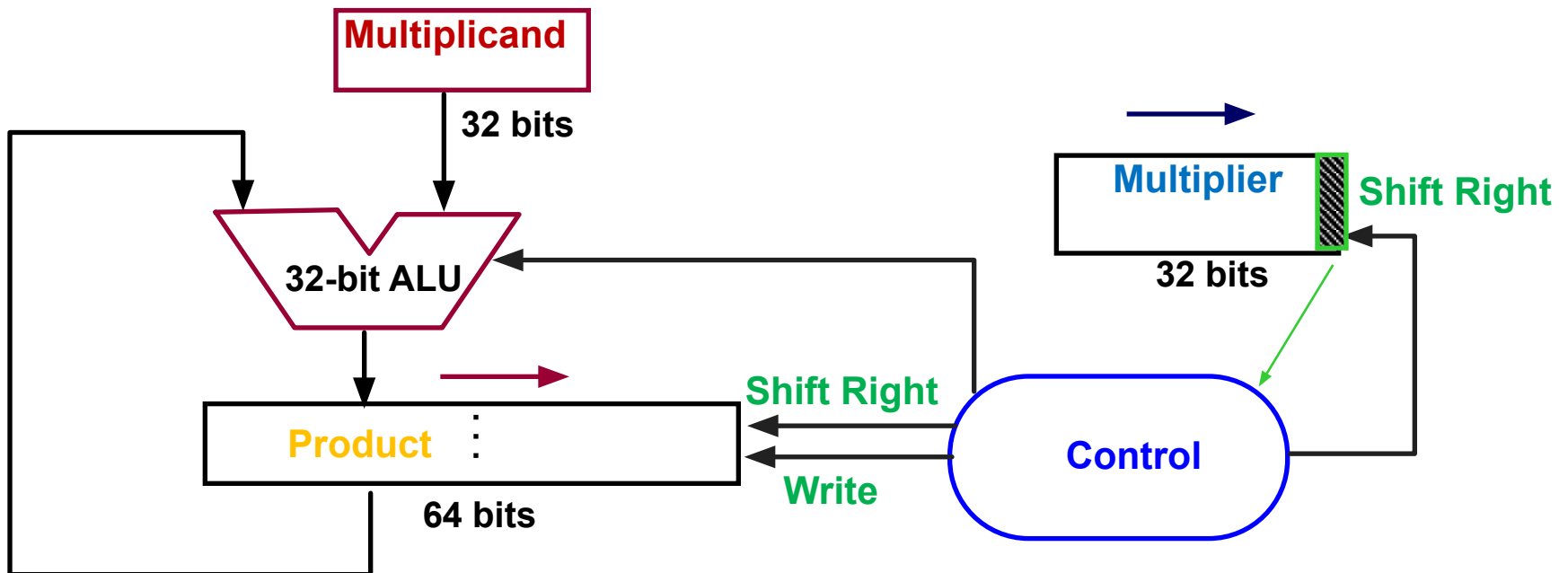

Multiply Algorithm Version 2

 

Multiplicand stays still
Product shifts right
Multiplier shifts right!

An Example

Follow the multiplication algorithm (version 2) to get the product of 2×3 using only 4-bit binary representation

Doesn't
Change




Iteration	Step	Multiplier	Multiplicand	Product
0	Initial value	0011	0010	0000 0000
1				
2				
3				
4				

Can we do something better?

Multiply Hardware Version 3

- Product register wastes space that exactly matches size of multiplier
⇒ combine Multiplier register and Product register
- Uses only 32-bit **Multiplicand** register, 32-bit ALU, 64-bit **Product** register, and 0-bit **Multiplier** register
- Shifting the product register would remove the least significant bit which is already used in the multiplication
- The most significant 32-bits are still being used by ALU as a result register

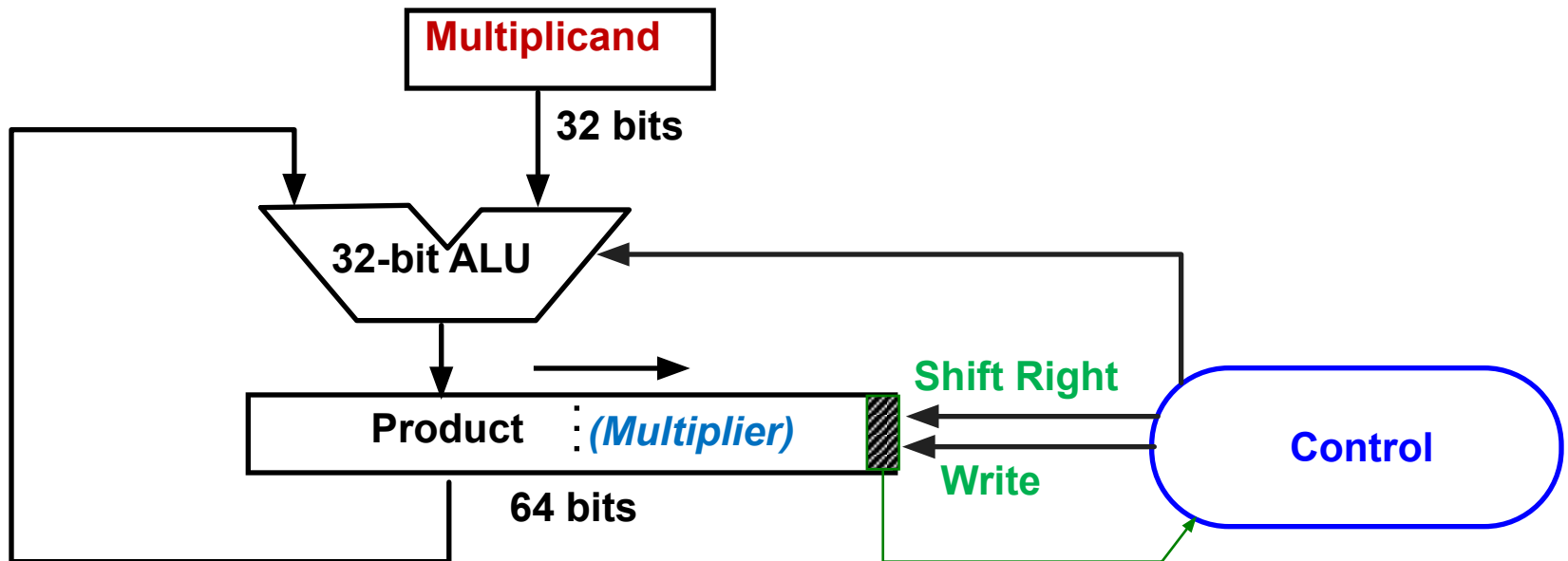


Multiply Algorithm Version 3

2 steps per bit because
Multiplier & Product combined

The product of 2×3

Iteration	Step	Multiplicand	Product
0	Initial value	0010	0000 0011
1			
2			
3			
4			

↑ ↑
MIPS registers Hi & Lo

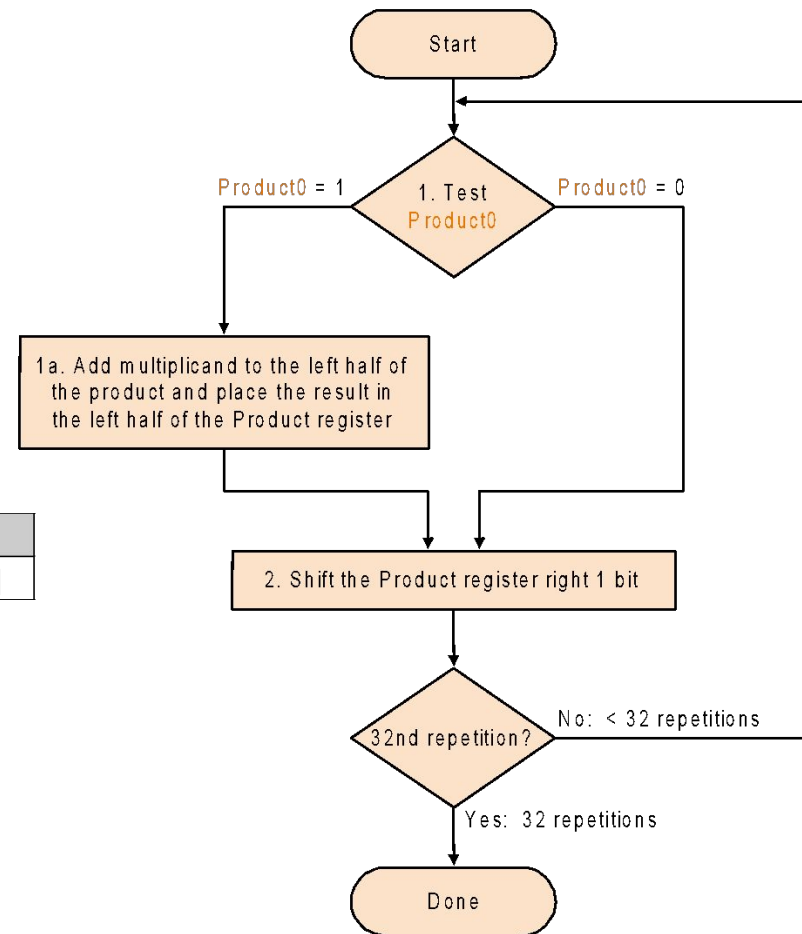

Multiplying Signed Number

- Easiest solution is to make both positive and remember whether to complement product when done (leave out the sign bit, run for 31 steps)
- Alternative idea: Apply definition of 2's complement \Rightarrow need to sign-extend partial products

Example: multiply 1001 (-7) by 0010 (+2)

Iteration	Step	Multiplicand	Product
0	Initial value	1001	0000 0010
1			
2			
3			
4			

$$-128 + (64 + 32 + 16 + 2) = -14$$

Does it work for all cases?

Multiply 0111 (+7) by 1110 (-2)

Iteration	Step	Multiplicand	Product
0	Initial value	0111	0000 1110
1	1a: 0 \Rightarrow no operation	0111	0000 1110
	2: Shift right Product	0111	0000 0111
2	1a: 1 \Rightarrow Prod = Prod + Mcand	0111	0111 0111
	2: Shift right Product	0111	0011 1011
3	1a: 0 \Rightarrow Prod = Prod + Mcand	0111	1010 1011
	2: Shift right Product	0111	1101 0101
4	1a: 0 \Rightarrow Prod = Prod + Mcand	0111	0100 0101
	2: Shift right Product	0111	0010 0010



Solution: Booth's Algorithm

An elegant way to multiply signed numbers using same hardware as before and save cycles

The Idea Behind Booth's Algorithm

Let's say we want to compute the following multiplication

$$1101 \times 0111$$

Since there are three 1's in 0111, normally this would require
3 “8-bit numbers addition” = 24 “1-bit addition”

How about writing the same multiplication in the following format?

$$1101 \times (1000-0001)$$

There are two 1's here, this would require
1 “8-bit numbers addition” and 1 “8-bit numbers subtraction”

Booth observed and proved that this can be partially
applied to multiplication of long binary numbers

Booth's Algorithm

Let's say we want to multiply M by $n = 6$

$$n = 6 = (0110)_2$$

$$\begin{aligned}\text{Product} &= M * (8 - 2) \\ &= (M * 8) - (M * 2) \\ &= (M * 2^3) - (M * 2^1) \\ &= \text{shifting M left by 3} - \text{shifting M left by 1}\end{aligned}$$

How can this be implemented on ALU? Booth came up with the following algo
Scan left from the LSB, compare current “bit i ” with the previous “bit $i-1$ ” to take the arithmetic action

- 00 \Rightarrow no arithmetic operation
- 01 \Rightarrow add multiplicand to left half of product
- 10 \Rightarrow subtract multiplicand from left half of product
- 11 \Rightarrow no arithmetic operation

Important: If it is the FIRST pass, use 0 as the previous LSB.

Binary Arithmetic

$$\begin{array}{cccccc}
 2^5 & 2^4 & 2^3 & 2^2 & 2^1 & 2^0 \\
 0 & 1 & 1 & 0 & 0 & 0
 \end{array}
 \Rightarrow 24 = 2^5 - 2^3 = 32 - 8$$

Starting from LSB, scan left

0 0 \Rightarrow no arithmetic operation

0 1 \Rightarrow add 2^i to the sum

1 0 \Rightarrow subtract 2^i from the sum

1 1 \Rightarrow no arithmetic operation

0010	2
x 0110	x 6
<hr/>	<hr/>

$$\begin{aligned}
 \text{Product} &= 2 * (8 - 2) \\
 &= (2 * 8) - (2 * 2) \\
 &= (0010 * 2^3) - (0010 * 2^1) \\
 &= (\text{shift } 0010 \text{ left by } 3) - (\text{shifting } 0010 \text{ left by } 1) \\
 &= 0001\ 0000 - 0000\ 0100 \\
 &= 0001\ 0000 + \underline{1111\ 1100} \quad (\text{2's complement of } 4)
 \end{aligned}$$

Booth's Algorithm

Why should we use Booth's Algorithm?

- Provides fast multiplication for consecutive 0's or 1's in the multiplier
- Handles signed multiplication
 - Extend the sign when shifting to preserve the sign (arithmetic right shift)

Example (unsigned numbers)

Compare the multiplication algorithm (version 3) and Booth's algorithm applied to getting the product of 2×6 using only 4-bit binary representation

Multiplicand	Original Algorithm		Booth's Algorithm	
	Step	Product	Step	Product
0010	Initial value	0000 0110	Initial value	0000 0110 0
0010	1a: 0 \Rightarrow no operation	0000 0110	1a: 00 \Rightarrow no operation	0000 0110 0
0010	2: Shift right Product	0000 0011	2: Shift right Product	0000 0011 0
0010	1a: 1 \Rightarrow Prod = Prod + Mcand	0010 0011	1a: 10 \Rightarrow Prod = Prod - Mcand	1110 0011 0
0010	2: Shift right Product	0001 0001	2: Shift right Product	1111 0001 1
0010	1a: 1 \Rightarrow Prod = Prod + Mcand	0011 0001	1a: 11 \Rightarrow no operation	1111 0001 1
0010	2: Shift right Product	0001 1000	2: Shift right Product	1111 1000 1
0010	1a: 0 \Rightarrow no operation	0001 1000	1a: 01 \Rightarrow Prod = Prod + Mcand	0001 1000 1
0010	2: Shift right Product	0000 1100	2: Shift right Product	0000 1100 0

- Booth's algorithm uses both the current bit and the previous bit to determine its course of action
- Extend the sign when shifting to preserve the sign (*arithmetic right shift*)

Example (signed numbers)

Follow Booth's algorithm to get the product of 2×-3 using only 4-bit binary representation


Iteration	Step	Multiplicand	Product
0	Initial value	0010	0000 1101 0
1	1a: 10 \Rightarrow Prod = Prod - Mcand	0010	1110 1101 0
	2: Shift right Product	0010	1111 0110 1
2	1a: 01 \Rightarrow Prod = Prod + Mcand	0010	0001 0110 1
	2: Shift right Product	0010	0000 1011 0
3	1a: 10 \Rightarrow Prod = Prod - Mcand	0010	1110 1011 0
	2: Shift right Product	0010	1111 0101 1
4	1a: 11 \Rightarrow no operation	0010	1111 0101 1
	2: Shift right Product	0010	1111 1010 1

Faster Multiplication-1

- We know whether the multiplicand is to be added or not at the beginning of the multiplication by looking at each of the 32 multiplier bits
- Faster multiplications are possible by essentially providing **one 32-bit adder for each bit of the multiplier**
 - Input-1: the **multiplicand** **AND**ed with a **multiplier bit**
 - Input-2: the output of a prior adder

Faster Multiplication-1

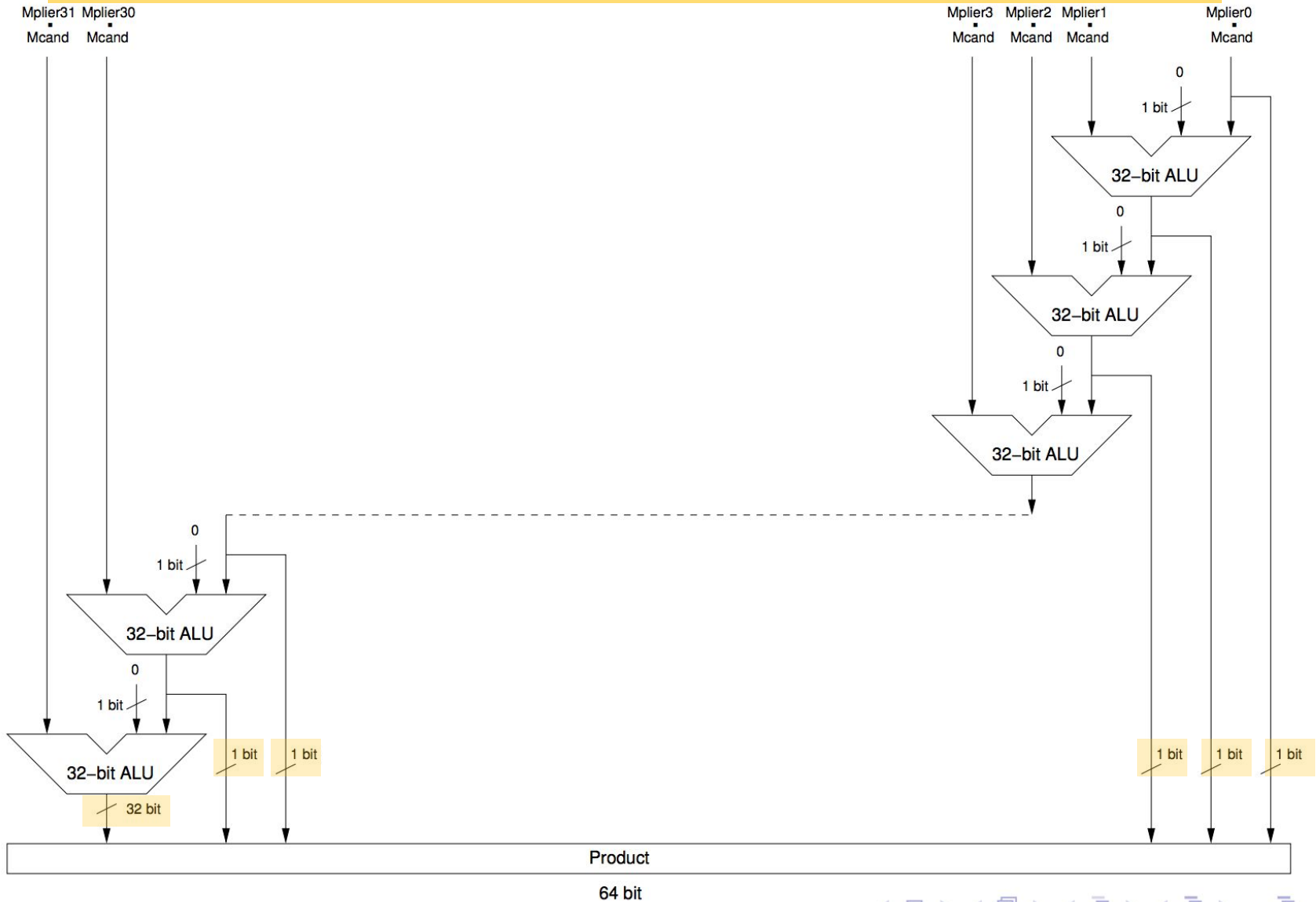Since we deal with bit-wise ANDs, no data storage is required



Faster Multiplication-2

